 



Basic Language Concepts

Describing Design Entities



- Primary programming abstraction is a *design entity*
 - Register, logic block, chip, board, or system
- What aspects of a digital system do we want to describe?
 - Interface: how do we connect to it
 - Function: what does it do?
- VHDL 1993 vs. VHDL 1987

 Describing the Interface: The Entity Construct



- The interface is a collection of *ports*
 - Ports are a new programming object: *signal*
 - Ports have a type, e.g., bit
 - Ports have a mode: in, out, inout (bidirectional)


(3)

The Signal Object Type

- VHDL supports four basic objects: variables, constants, signals and file types (1993)
- Variable and constant types
 - Follow traditional concepts
- The signal object type is motivated by digital system modeling
 - Distinct from variable types in the association of time with values
 - Implementation of a signal is a sequence of time-value pairs!
 - Referred to as the driver for the signal


(4)

Example Entity Descriptions

 

```
entity ALU32 is
port(
  A, B: in bit_vector (31 downto 0);
  C : out bit_vector (31 downto 0);
  Op: in bit_vector (5 downto 0);
  N, Z: out bit);
end entity ALU32;
```


MSB LSB

 

```
entity D_ff is
port(
  D, Q, Clk, R, S: in bit;
  Q, Qbar : out bit);
end entity D_ff;
```

 (5)

Describing Behavior: The Architecture Construct



```
entity half_adder is
port (a, b : in bit;
      sum, carry :out bit);
end entity half_adder;


architecture behavioral of half_adder is
begin
  sum <= (a xor b) after 5 ns;
  carry <= (a and b) after 5 ns;
end architecture behavior;
```

VHDL 1993


- Description of events on output signals in terms of events on input signals: the *signal assignment* statement
- Specification of propagation delays
- Type **bit** is not powerful enough for realistic simulation: use the IEEE 1164 value system

(6)

Example Entity Descriptions: IEEE 1164

 

 
```
entity ALU32 is
  port(
    A, B: in std_ulogic_vector (31 downto 0);
    C : out std_ulogic_vector (31 downto 0);
    Op: in std_ulogic_vector (5 downto 0);
    N, Z: out std_logic);
end entity ALU32;
```



```
entity D_ff is
  port(
    D, Q, Clk, R, S: in std_ulogic;
    Q, Qbar : out std_ulogic);
end entity D_ff;
```

 (7)

Describing Behavior: The Architecture Construct



```
library IEEE;
use IEEE.std_logic_1164.all;
```

} Declarations for a design entity

```
entity half_adder is
  port (a, b : in std_ulogic;
        sum, carry : out std_ulogic);
end entity half_adder;
```


```
architecture behavioral of half_adder is
begin
  sum <= (a xor b) after 5 ns;
  carry <= (a and b) after 5 ns;
end architecture behavioral;
```

- Use of the IEEE 1164 value system requires inclusion of the library and package declaration statements

 (8)


Libraries and Packages

- Libraries are logical units that are mapped to physical directories
- Packages are repositories for type definitions, procedures, and functions
 - User defined vs. system packages



(9)

Configurations

 

- Separate the specification of the interface from that of the implementation
 - An entity may have multiple architectures
- Configurations associate an entity with an architecture
 - Binding rules: default and explicit
- Use configurations (more later!)

(10)

- *Primary* design units
 - Entity
 - Configuration
 - Package Declaration
 - These are not dependent on other design units
- *Secondary* design units
 - Package body
 - Architecture
- Design units are created in design files
- Now you know the layout of a VHDL program!


(11)

Simple Signal Assignment

```
library IEEE;
use IEEE.std_logic_1164.all;
entity full_adder is
port (in1, in2, c_in: in std_logic;
      sum, c_out: out std_logic);
end entity full_adder;
```

```
architecture dataflow of full_adder is
  signal s1, s2, s3 : std_logic;
  constant gate_delay: Time := 5 ns;
begin
  L1: s1 <= (in1 xor in2) after gate_delay;
  L2: s2 <= (c_in and s1) after gate_delay;
  L3: s3 <= (in1 and in2) after gate_delay;
  L4: sum <= (s1 xor c_in) after gate_delay;
  L5: c_out <= (s2 or s3) after gate_delay;
end architecture dataflow;
```

} Declarations

 


(12)

Simple Signal Assignment Statement

- The *constant* programming object
 - Values cannot be changed
- Use of *signals* in the architecture
 - Internal signals connect components
- A statement is executed when an event takes place on a signal in the RHS of an expression
 - 1-1 correspondence between signal assignment statements and signals in the circuit
 - Order of statement execution follows propagation of events in the circuit
 - Textual order **does not** imply execution order

(13)

Implementation of Signals

 

(14)




Implementation of Signals (cont.)

- In the absence of initialization, default values are determined by signal type
- Waveform elements describe time-value pairs
- *Transactions* are internal representations of signal value assignments
 - Events correspond to new signal values
 - A transaction may lead to the same signal value

(15)




Implementation of Signals (cont.)

 

- *Driver* is set of future signal values: current signal value is provided by the transaction at the head of the list
- We can specify multiple waveform elements in a single assignment statement
 - Specifying multiple future values for a signal
- Rules for maintaining the driver
 - Conflicting transactions

(16)

Example: Waveform Generation

 


signal <= '0','1' after 10 ns,'0' after 20 ns,'1' after 40 ns;

- Multiple waveform elements can be specified in a single signal assignment statement
- Describe the signal transitions at future point in time
 - Each transition is specified as a waveform element

(17)

Resolved Signal Types

 

- At any point in time what is the value of the bus signal?
- We need to “resolve” the value
 - Take the value at the head of all drivers
 - Select one of the values according to a resolution function
- Predefined IEEE 1164 resolved types are std_logic and std_logic_vector

(18)

Conditional Signal Assignment

```

library IEEE;
use IEEE.std_logic_1164.all;
entity mux4 is
port ( In0, In1, In2, In3 : in std_logic_vector (7 downto 0);
Sel: in std_logic_vector(1 downto 0);
Z : out std_logic_vector (7 downto 0));
end entity mux4;
architecture behavioral of mux4 is
begin
Z <= In0 after 5 ns when Sel = "00" else
In1 after 5 ns when Sel = "01" else
In2 after 5 ns when Sel = "10" else
In3 after 5 ns when Sel = "11" else
"00000000" after 5 ns;
end architecture behavioral;

```

note type

← Evaluation Order is important!

- First true conditional expression determines the output value

(19)

Unaffected Signals

```

library IEEE;
use IEEE.std_logic_1164.all;
entity pr_encoder is
port (S0, S1, S2, S3: in std_logic;
Z : out std_logic_vector (1 downto 0));
end entity pr_encoder;
architecture behavioral of pr_encoder is
begin
Z <= "00" after 5 ns when S0 = '1' else
"01" after 5 ns when S1 = '1' else
unaffected when S2 = '1' else
"11" after 5 ns when S3 = '1' else
"00" after 5 ns;
end architecture behavioral;

```

- Value of the signal is not changed
- VHDL 1993 only!

(20)



Selected Signal Assignment Statement

```
library IEEE;
use IEEE.std_logic_1164.all;
entity mux4 is
port ( In0, In1, In2, In3 : in std_logic_vector (7 downto 0);
Sel: in std_logic_vector(1 downto 0);
Z : out std_logic_vector (7 downto 0));
end entity mux4;
architecture behavioral-2 of mux4 is
begin
with Sel select
Z <= (In0 after 5 ns) when "00",
(In1 after 5 ns) when "01",
(In2 after 5 ns) when "10",
(In3 after 5 ns) when "11",
(In3 after 5 ns) when others;
end architecture behavioral;
```

← All options must be covered
and only one
must be true!

- The "when others" clause can be used to ensure that all options are covered
- The "unaffected" clause may also be used here

(21)



A VHDL Model Template

```
library library-name-1, library-name-2;
use library-name-1.package-name.all;
use library-name-2.package-name.all;
```

} Declare external libraries and
visible components

```
entity entity_name is
port(   input signals : in type;
       output signals : out type);
end entity entity_name;
```

} Define the interface

```
architecture arch_name of entity_name is
-- declare internal signals
-- you may have multiple signals of different types
signal internal-signal-1 : type := initialization;
signal internal-signal-2 : type := initialization;
```

} Declare signals used to connect
components

```
begin
-- specify value of each signal as a function of other signals
internal-signal-1 <= simple, conditional, or selected CSA;
internal-signal-2 <= simple, conditional, or selected CSA;
```

} Definition of how & when *internal*
signal values are computed

```
output-signal-1 <= simple, conditional, or selected CSA;
output-signal-2 <= simple, conditional, or selected CSA;
end architecture arch_name;
```

} Definition of how & when *external*
signal values are computed


(22)

Delay Models in VHDL

- Inertial delay
 - Default delay model
 - Suitable for modeling delays through devices such as gates
- Transport Delay
 - Model delays through devices with very small inertia, e.g., wires
 - All input events are propagated to output signals
- Delta delay
 - What about models where no propagation delays are specified?
 - Infinitesimally small delay is automatically inserted by the simulator to preserve correct ordering of events

(23)

Inertial Delays: Example

 


- *signal* <= **reject** *time-expression* **inertial** *value-expression* **after** *time-expression*;
- Most general form of a waveform element
- VHDL 1993 enables specification of pulse rejection width

(24)

Transport Delays: Example

```

 architecture transport_delay of half_adder is
  signal s1, s2: std_logic := '0';
  begin
    s1 <= (a xor b) after 2 ns;
    s2 <= (a and b) after 2 ns;
    sum <= transport s1 after 4 ns;
    carry <= transport s2 after 4 ns;
  end architecture transport_delay;
  
```



(25)


Delta Delays: Example

```

library IEEE;
  use IEEE.std_logic_1164.all;
  entity combinational is
    port (In1, In2: in std_logic;
          z: out std_logic);
  end entity combinational;
  
```


```

 architecture behavior of combinational
  signal s1, s2, s3, s4: std_logic := '0';
  begin
    s1 <= not In1;
    s2 <= not In2;
    s3 <= not (s1 and In2);
    s4 <= not (s2 and In1);
    z <= not (s3 and s4);
  end architecture behavior;
  
```



(26)

Delta Delays: Behavior

 

(27)

Delay Models: Summary

- Delay models
 - Inertial
 - For devices with inertia such as gates
 - VHDL 1993 supports pulse rejection widths
 - Transport
 - Ensures propagation of all events
 - Typically used to model elements such as wires
 - Delta
 - Automatically inserted to ensure functional correctness of code blocks that do not specify timing
 - Enforces the data dependencies specified in the code

(28)

- Primary unit of abstraction is a design entity
- Design units include
 - Primary design units
 - entity, configuration, package declaration
 - Secondary design units
 - architecture, package body
- Concurrent signal assignment statements
 - Simple, selected, conditional
 - Can be coalesced to form models of combinational circuits