 



# Modeling Structure

## Elements of Structural Models



- Structural models describe a digital system as an interconnection of components
- Descriptions of the behavior of the components must be independently available as structural or behavioral models
  - An entity/architecture for each component must be available

## Modeling Structure

 

- Define the components used in the design
- Describe the interconnection of these components

(3)

## Modeling Structure

```

architecture structural of full_adder is
  component half_adder is -- the declaration
    port (a, b : in std_logic; -- of components you will use
          sum, carry: out std_logic);
  end component half_adder;
  component or_2 is
    port(a, b : in std_logic;
          c : out std_logic);
  end component or_2;
  signal s1, s2, s3 : std_logic;
begin
  H1: half_adder port map (a => In1, b => In2, sum=>s1, carry=>s3);
  H2: half_adder port map (a => s1, b => c_in, sum =>sum,
    carry => s2);
  O1: or_2 port map (a => s2, b => s3, c => c_out);
end architecture structural;

```

Annotations:

- unique name of the components (points to H1, H2, O1)
- component type (points to half\_adder, or\_2)
- interconnection of the component (points to the port map statements)
- ports (points to the port declarations)
- component instantiation statement (points to the port map statements)

- Entity/architecture for *half\_adder* and *or\_2* must exist

(4)



## Example: State Machine

```
library IEEE;
use IEEE.std_logic_1164.all;
entity serial_adder is
port (x, y, clk, reset : in std_logic;
      z : out std_logic);
end entity serial_adder;
architecture structural of serial_adder is
--
-- declare the components that we will be using
--
component comb is
port (x, y, c_in : in std_logic;
      z, carry : out std_logic);
end component comb;

component dff is
port (clk, reset, d : in std_logic;
      q, qbar : out std_logic);
end component dff;
signal s1, s2 : std_logic;
begin
--
-- describe the component interconnection
--
C1: comb port map (x => x, y => y, c_in =>
s1, z => z, carry => s2);
D1: dff port map (clk => clk, reset => reset,
d => s2, q => s1,
qbar => open);
end architecture structural;
```

- Structural models can be easily generated from schematics
- Name conflicts in the association lists?
- The “open” attribute

(5)




## Hierarchy and Abstraction

```
architecture structural of half_adder is
component xor2 is
port (a, b : in std_logic;
      c : out std_logic);
end component xor2;
component and2 is
port (a, b : in std_logic;
      c : out std_logic);
end component and2;
begin
EX1: xor2 port map (a => a, b => b, c => sum);
AND1: and2 port map (a => a, b => b, c => carry);
end architecture structural;
```

- Structural descriptions can be nested
- The half adder may itself be a structural model

(6)


## Hierarchy and Abstraction

 

- Nested structural descriptions to produce hierarchical models
- The hierarchy is flattened prior to simulation
- Behavioral models of components at the bottom level must exist

(7)

## Hierarchy and Abstraction

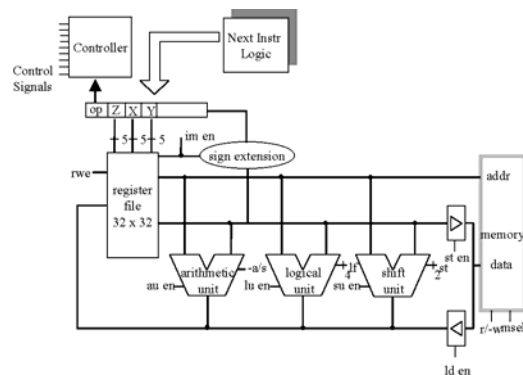

- Use of IP cores and vendor libraries
- Simulations can be at varying levels of abstraction for individual components

(8)

```

library IEEE;
use IEEE.std_logic_1164.all;

entity xor2 is
  generic (gate_delay : Time:= 2 ns);
  port(In1, In2 : in std_logic;
    z : out std_logic);
end entity xor2;

architecture behavioral of xor2 is
  begin
    z <= (In1 xor In2) after gate_delay;
  end architecture behavioral;

```

- Enables the construction of parameterized models

(9)

## Generics in Hierarchical Models

```



architecture generic_delay of half_adder is
  component xor2
    generic (gate_delay: Time);
    port (a, b : in std_logic;
      c : out std_logic);
  end component;
  component and2
    generic (gate_delay: Time);
    port (a, b : in std_logic;
      c : out std_logic);
  end component;
  begin
    EX1: xor2 generic map (gate_delay => 6 ns)
      port map(a => a, b => b, c => sum);
    A1: and2 generic map (gate_delay => 3 ns)
      port map(a=> a, b=> b, c=> carry);
  end architecture generic_delay;

```

- Parameter values are passed through the hierarchy


(10)

## Example: Full Adder

  

(11)

## Example: Full Adder

 

(12)

## Precedence of Generic Declarations

```

architecture generic_delay2 of half_adder is
  component xor2
    generic (gate_delay: Time);
    port(a,b : in std_logic;
        c : out std_logic);
  end component;

  component and2
    generic (gate_delay: Time:= 6 ns);
    port (a, b : in std_logic;
        c : out std_logic);
  end component;


  begin
    EX1: xor2 generic map (gate_delay => gate_delay)
    port map(a => a, b => b, c => sum);
    A1: and2 generic map (gate_delay => 4 ns)
    port map(a=> a, b=> b, c=> carry);
  end generic_delay2;
  
```

→ *takes precedence*

- Generic map takes precedence over the component declaration

(13)

## Generics: Properties

 

- Generics are constant objects and can only be read
- The values of generics must be known at compile time
- They are a part of the interface specification but do not have a physical interpretation
- Use of generics is not limited to "delay like" parameters and are in fact a very powerful structuring mechanism

(14)

## Example: N-Input Gate

```

entity generic_or is
generic (n: positive:=2);
port (in1 : in std_logic_vector ((n-1) downto 0);
      z : out std_logic);
end entity generic_or;
architecture behavioral of generic_or is
begin
  process (in1) is
    variable sum : std_logic:= '0';
  begin
    sum := '0'; -- on an input signal transition sum must
                be reset
    for i in 0 to (n-1) loop
      sum := sum or in1(i);
    end loop;
    z <= sum;
  end process;
end architecture behavioral;

```

- Map the generics to create different size OR gates

(15)

## Example: Using the Generic N-Input OR Gate

```

architecture structural of full_adder is
  component generic_or
    generic (n: positive);
    port (in1 : in std_logic_vector ((n-1) downto 0);
          z : out std_logic);
  end component;
  ...
  ... -- remainder of the declarative region from earlier example
  ...
begin
  H1: half_adder      port map (a => In1, b => In2, sum=>s1, carry=>s3);
  H2:half_adder      port map (a => s1, b => c_in, sum =>sum, carry => s2);
  O1: generic_or      generic map (n => 2)
                      port map (a => s2, b => s3, c => c_out);
end structural;

```

- Full adder model can be modified to use the generic OR gate model via the *generic map ()* construct
- Analogy with macros

(16)



## Example: N-bit Register

```
entity generic_reg is
  generic (n: positive:=2);
  port (   clk, reset, enable : in std_logic;
         d : in std_logic_vector (n-1 downto 0);
         q : out std_logic_vector (n-1 downto 0));
end entity generic_reg;
architecture behavioral of generic_reg is
begin
  reg_process: process (clk, reset)
  begin
    if reset = '1' then
      q <= (others => '0');
    elsif (rising_edge(clk)) then
      if enable = '1' then q <= d;
      end if;
    end if;
  end process reg_process;
end architecture behavioral;
```

- This model is used in the same manner as the generic OR gate

(17)

## Component Instantiation and Synthesis

- Design methodology for inclusion of highly optimized components or “cores”
  - Optimized in the sense of placed and routed
  - Intellectual property cores for sale
  - Check out <http://www.xilinx.com/ipcenter/index.htm>
- Core generators for static generation of cores
  - Generation of VHDL/Verilog models of placed and routed designs
  - Component instantiation for using cores in a design
- Access to special components/circuitry within the target chip

(18)



## Example: Using Global Resources

```

library IEEE;
use IEEE.std_logic_1164.all;

entity my_clocks is
port (phi1, phi2: out std_logic);
end entity my_clocks;

architecture behavioral of my_clocks is
component OSC4 is -- on chip oscillator
port (F8M : out std_logic; -- 8 Mhz clock
F500k : out std_logic;-- 500Khz clock
F15 : out std_logic);-- 15 hz clock
end component OSC4;

component BUFG is -- global buffer connection
to low skew lines
port (I : in std_logic;
O : out std_logic);
end component BUFG;

signal local_F15, local_phi2 : std_logic; -- local
signals

begin
O1: osc4 port map(F15 =>local_F15); --
instantiate the oscillator
B1: bufg port map (I => local_F15, O => phi1); --
instantiate the two global buffers
B2: bufg port map (I => local_phi2, O => phi2);

local_phi2 <= not local_F15; -- phi2 is the
complement of phi1

end architecture behavioral;

```

- Component abstractions for special support within the chip
  - For global signals
  - For shared system level components

(19)



## Implementing Global Set/Reset in VHDL

```

library IEEE;
use IEEE.std_logic_1164.all;

entity sig_var is
port ( clk, reset,x, y, z: in std_logic;
w : out std_logic);
end sig_var;

architecture behavior of sig_var is
component STARTUP is
port (GSR : in std_logic);
end component STARTUP;
signal s1, s2 : std_logic;
begin
U1: STARTUP port map(GSR => reset);

process
begin
wait until (rising_edge(clk));
if (reset = '1') then
w <= '0';
s1 <= '0';
s2 <= '0';
else
L1: s1 <= x xor y;
L2: s2 <= s1 or z;
L3: w <= s1 nor s2;
end if;
end process;
end behavior;

```

- GSR inferencing optimization
- Connect your reset signal to this global net
- Note
  - improves “routability” of designs

(20)

- Xilinx Logic Core utility
- Parameterized modules
  - User controlled generation of VHDL modules
  - Instantiation within a design
  - Simulator and synthesis
- Third party view of the world of hardware design
  - Analogy with software and compilers
  - What is software vs. hardware anymore?

(21)

- What if we need to instantiate a large number of components in a regular pattern?
  - Need conciseness of description
  - Iteration construct for instantiating components!
- The *generate* statement
  - A parameterized approach to describing the regular interconnection of components

**a: for i in 1 to 6 generate**

a1: one\_bit **generic map** (gate\_delay)

**port map**(in1=>in1(i), in2=> in2(i), cin=>carry\_vector(i-1),

result=>result(i), cout=>carry\_vector(i),opcode=>opcode);

**end generate;**

(22)



## The Generate Statement: Example

- Instantiating an register

```
entity dregister is
port ( d : in std_logic_vector(7 downto 0);
      q : out std_logic_vector(7 downto 0);
      clk : in std_logic);
end entity dregisters
architecture behavioral of dregister is
begin
  d: for i in dreg'range generate
    reg: dff port map( (d=>d(i), q=>q(i), clk=>clk);
  end generate;
end architecture register;
```

- Instantiating interconnected components
  - Declare local signals used for the interconnect

(23)



## The Generate Statement: Example

```
library IEEE;
use IEEE.std_logic_1164.all;

entity multi_bit_generate is
generic(gate_delay:time:= 1 ns;
        width:natural:=8); -- the default is a 8-bit ALU
port( in1 : in std_logic_vector(width-1 downto 0);
      in2 : in std_logic_vector(width-1 downto 0);
      result : out std_logic_vector(width-1 downto 0);
      opcode : in std_logic_vector(1 downto 0);
      cin : in std_logic;
      cout : out std_logic);
end entity multi_bit_generate;

architecture behavioral of multi_bit_generate is

  component one_bit is -- declare the single bit ALU
    generic (gate_delay:time);
    port (in1, in2, cin : in std_logic;
          result, cout : out std_logic;
          opcode: in std_logic_vector (1 downto 0));
  end component one_bit;

  signal carry_vector: std_logic_vector(width-2 downto 0);
  -- the set of signals for the ripple carry

begin
  a0: one_bit generic map (gate_delay) -- instantiate ALU
  for bit position 0
    port map (in1=>in1(0), in2=>in2(0), result=>result(0),
              cin=>cin, opcode=>opcode, cout=>carry_vector(0));

  a2to6: for i in 1 to width-2 generate -- generate
  instantiations for bit positions 2-6
    a1: one_bit generic map (gate_delay)
    port map (in1=>in1(i), in2=> in2(i), cin=>carry_vector(i-1),
              result=>result(i), cout=>carry_vector(i),opcode=>opcode);
  end generate;

  a7: one_bit generic map (gate_delay) -- instantiate ALU
  for bit position 7
    port map (in1=>in1(width-1), in2=>in2(width-1), result=>
              result(width-1), cin=>carry_vector(width-2),
              opcode=>opcode, cout=>cout);
  end architecture behavioral;
```


(24)

## Using the Generate Statement

- Identify components with regular interconnect
- Declare local arrays of signals for the regular interconnections
- Write the generate statement
  - Analogy with loops and multidimensional arrays
  - Beware of unconnected signals!
- Instantiate remaining components of the design

(25)


## Configurations

 

- A design entity can have multiple alternative architectures
- A configuration specifies the architecture that is to be used to implement a design entity

(26)

## Component Binding

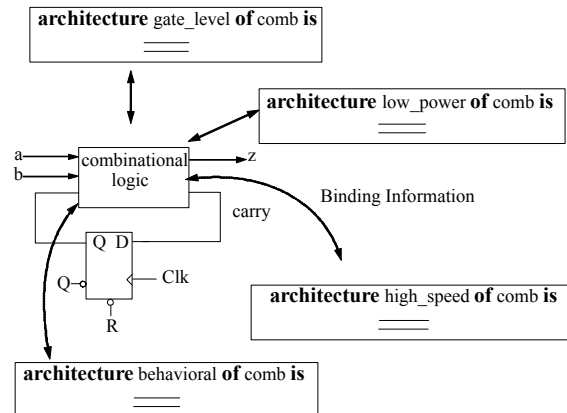

- We are concerned with configuring the architecture and not the entity
- Enhances sharing of designs: simply change the configuration

(27)

## Default Binding Rules

```
architecture structural of serial_adder is
  component comb is
  port (a, b, c_in : in std_logic;
        z, carry : out std_logic);
  end component comb;
```

```
component dff is
  port (clk, reset, d : in std_logic;
        q, qbar : out std_logic);
  end component dff;
signal s1, s2 : std_logic;
```

```
begin
  C1: comb port map (a => a, b => b, c_in => s1, z => z, carry => s2);
  D1: dff port map (clk => clk, reset => reset, d => s2, q => s1, qbar => open);
end architecture structural;
```

- Search for entity with the same component name
- If multiple such entities exist, bind the last compiled architecture for that entity
- How do we get more control over binding?

(28)

## Configuration Specification

**architecture** structural of full\_adder is

--

--declare components here

**signal** s1, s2, s3: std\_logic;

--

-- configuration specification

**for** H1: half\_adder **use entity** WORK.half\_adder (behavioral);

**for** H2: half\_adder **use entity** WORK.half\_adder (structural);

**for** O1: or\_2 **use entity** POWER.lpo2 (behavioral)

**generic map**(gate\_delay => gate\_delay)

**port map** (I1 => a, I2 => b, Z=>c);

**begin** -- component instantiation statements

H1: half\_adder **port map** (a => In1, b => In2, sum => s1, carry=> s2);

H2: half\_adder **port map** (a => s1, b => c\_in, sum => sum, carry => s2);

O1: or\_2 **port map**(a => s2, b => s3, c => c\_out);

**end** structural;

library name  
entity name  
architecture name

- We can *specify* any binding where ports and arguments match

(29)

## Configuration Specification

- Short form where applicable  
**for all:** half\_adder **use entity** WORK.half\_adder (behavioral);
- Not constrained by the name space
- Delayed binding when a specification is not present
  - Will be available at a later step
  - Analogous to unresolved symbol references during compilation of traditional programs

(30)

## Configuration Declaration

```

configuration Config_A of full_adder is -- name the configuration
  -- for the entity
  for structural -- name of the architecture being configured
    for H1: half_adder use entity WORK.half_adder (behavioral);
    end for;
    --
    for H2: half_adder use entity WORK.half_adder (structural);
    end for;
    --
    for O1: or_2 use entity POWER.lpo2 (behavioral)
      generic map(gate_delay => gate_delay)
      port map (I1 => a, I2 => b, Z=>c);
    end for;
    --
  end for;
end Config_A;
  
```

- Written as a separate design unit
- Can be written to span a design hierarchy
- Use of the “for all” clause

(31)

## Summary

- Structural models
  - Syntactic description of a schematic
- Hierarchy and abstraction
  - Use of IP cores
  - Mixing varying levels of detail across components
- Generics
  - Construct parameterized models
  - Use in configuring the hardware
- Configurations
  - Configuration specification
  - Configuration declaration

(32)